

# CHAPTER 8

---

## Combinational Circuit design and Simulation Using Gate

# Contents

---

- 8.1 Review of Combinational Circuit Design
- 8.2 Design of Circuits with Limited Gate Fan-in
- 8.3 Gate delays and Timing Diagrams
- 8.4 Hazards in Combinational Logic
- 8.5 Simulation and Testing of Logic Circuits

# Objectives

---

**Topics introduced in this chapter:**

- **Draw a timing diagram for a combinational circuit with gate delays.**
- **Define static 0-and 1-hazards and dynamic hazard. Given a combinational circuit, find all of the static 0-and 1-hazards. For each hazard,specify the order in which the gate outputs must switch in order for the hazard to actually produce a false output.**
- **Given switching function, realize it using a two-level circuit which is free of static and dynamic hazards (for single input variable changes).**
- **Design a multiple-output NAND or NOR circuit using gates with limited fan-in.**
- **Explain the operation of a logic simulator that uses four-valued logic.**
- **Test and debug a logic circuit design using a simulator.**

## 8.2 Design of Circuits with Limited Gate Fan-in

Example: Realize  $f(a,b,c,d) = \sum m(0,3,4,5,8,9,10,14,15)$  using 3-input NOR gate

map of  $f$ :

$ab \backslash cd$	00	01	11	10
00	1	1	0	1
01	0	1	0	1
11	1	0	1	0
10	0	0	1	1


$$f' = a'b'c'd + ab'cd + abc' + a'bc + a'cd'$$

## 8.2 Design of Circuits with Limited Gate Fan-in

---

$$f' = b'd(a'c' + ac) + a'c(b + d' + abc')$$
 
$$f = [b + d' + (a + c)(a' + c')][a + c' + b'd][a' + b' + c]$$



## 8.2 Design of Circuits with Limited Gate Fan-in


Example: Realize the functions given in Figure 8-2,  
using only 2-input NAND gates and inverters.

If we minimize each function separately, the result is


$$f_1 = b'c' + ab' + a'b$$

$$f_2 = b'c' + bc + a'b$$


$$f_3 = a'b'c + ab + bc'$$

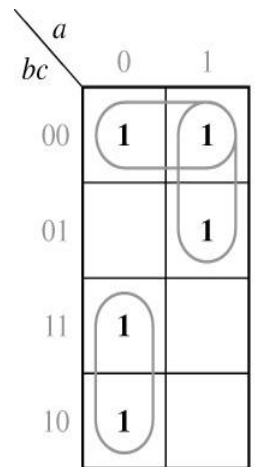

$$f_1 = \Sigma m(0, 2, 3, 4, 5)$$

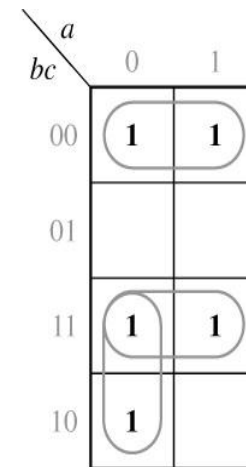

$$f_2 = \Sigma m(0, 2, 3, 4, 7)$$

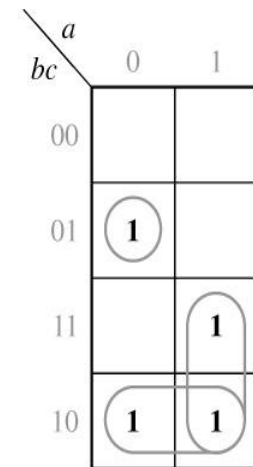

$$f_3 = \Sigma m(1, 2, 6, 7)$$

Figure 8-2

## 8.2 Design of Circuits with Limited Gate Fan-in

 


Figure 8-3: Realization of Figure 8-2

$$f_1 = b'(\underline{a'+c'}) + \underline{a'b}$$

$$f_2 = b(a'+c) + \underline{b'c'}$$



$$f_3 = a'b'c + b(\underline{a+c'})$$

$$f_2 = (b'+c)(b+c') + \underline{a'b}$$

$$a'b'c = a'(b'c) = a'(b+c')'$$

## 8.3 Gate Delays and Timing Diagrams



### Propagation Delay in an Inverter

  




## 8.3 Gate Delays and Timing Diagrams

### Timing Diagram for AND-NOR Circuit

  


## 8.3 Gate Delays and Timing Diagrams
 
### Timing Diagram for Circuit with Delay




## 8.4 Hazards in Combinational Logic

---

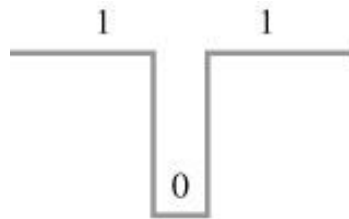

(a) Static 1-hazard

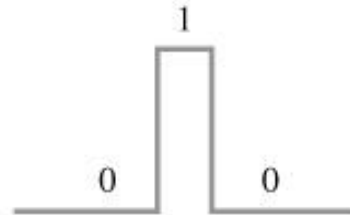

(b) Static 0-hazard




(c) Dynamic hazards


Types of Hazards

## 8.4 Hazards in Combinational Logic

### Detection of a 1-Hazard

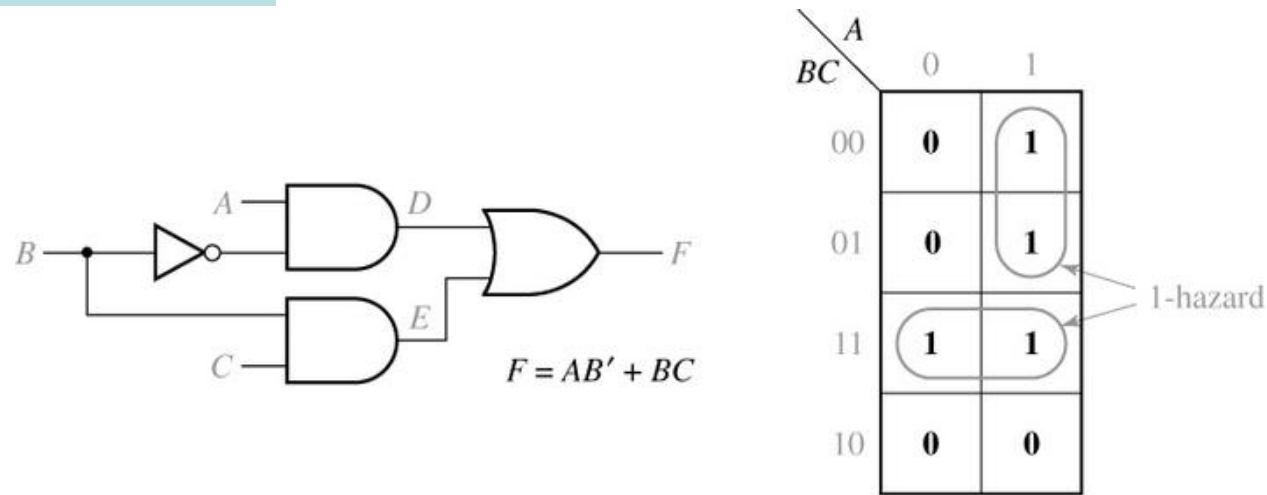


(a) Circuit with a static 1-hazard

 

(b) Timing chart

## 8.4 Hazards in Combinational Logic

Circuit with Hazard Removed

 


		A	
		0	1
BC	00	0	1
	01	0	1
	11	1	1
	10	0	0


## 8.4 Hazards in Combinational Logic

### Detection of a Static 0-Hazard


$$F = (A + C)(A' + D')(B' + C' + D)$$

 

(a) Circuit with a static 0-hazard

 


(b) Karnaugh map for circuit of (a)

 

(c) Timing diagram illustrating 0-hazard of (a)

## 8.4 Hazards in Combinational Logic


### Karnaugh Map Removing Hazards

 


$$F = (A + C)(A' + D')(B' + C' + D)(C + D')(A + B' + D)(A' + B' + C')$$

## 8.5 Simulation and Testing of Logic Circuit

---

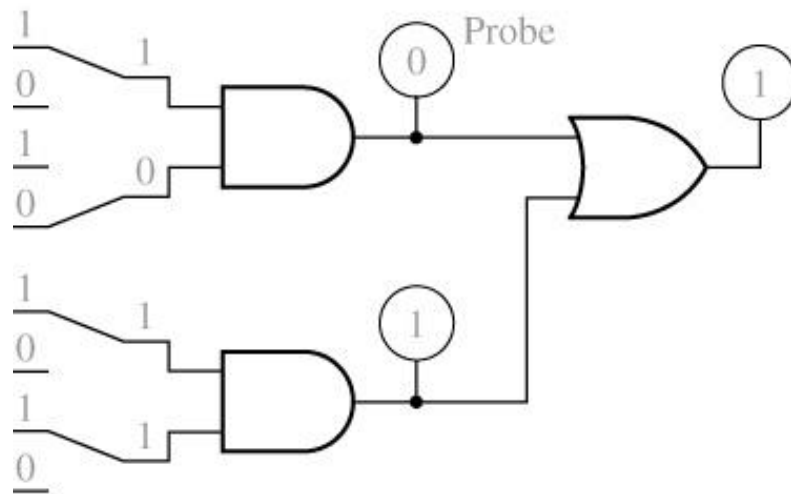

(a) Simulation screen showing switches

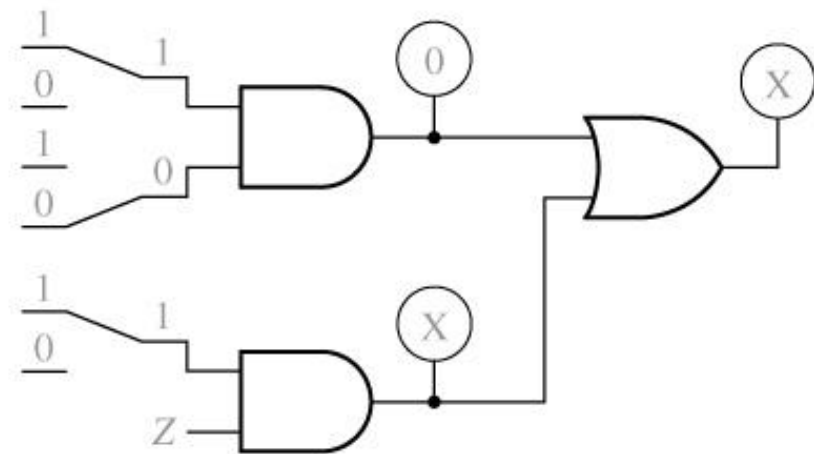

(b) Simulation screen with missing gate input



## 8.5 Simulation and Testing of Logic Circuit

### And and OR Functions for Four-Valued Simulation

·	0	1	X	Z
0	0	0	0	0
1	0	1	X	X
X	0	X	X	X
Z	0	X	X	X

+	0	1	X	Z
0	0	1	X	X
1	1	1	1	1
X	X	1	X	X
Z	X	1	X	X

## 8.5 Simulation and Testing of Logic Circuit

### Logic Circuit with Incorrect Output

Example:  $F = AB(C'D + CD') + A'B'(C + D)$

