

CENG-232

Logic Design


Lecture 3

Combinational Logic Design

Spring 2015 - Uluç Saranlı
saranli@ceng.metu.edu.tr

Combinational Logic

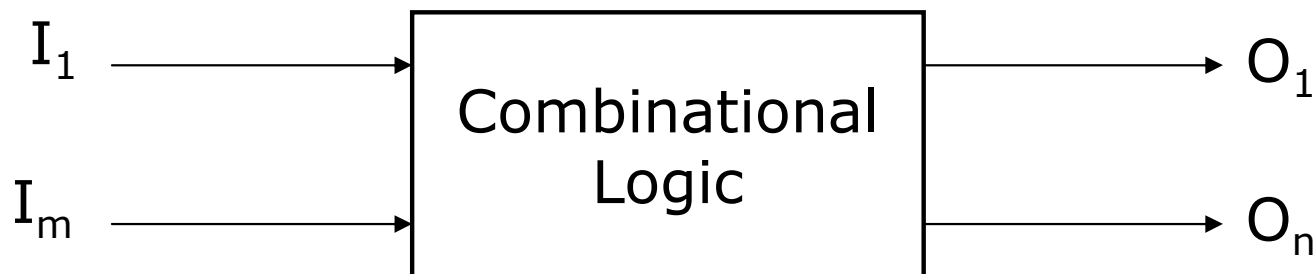- ▶ One or more digital signal inputs
- ▶ One or more digital signal outputs
- ▶ Outputs are only functions of current input values (ideal) plus logic propagation delays



$$\begin{aligned} O_1(t + \Delta t) &= F_1(I_1(t), \dots, I_m(t)) \\ &\vdots \\ O_n(t + \Delta t) &= F_n(I_1(t), \dots, I_m(t)) \end{aligned}$$

Combinational Logic (Cont'd.)

- ▶ **Combinational logic has no memory!**
 - ▶ Outputs are only function of current input combination
 - ▶ Nothing is known about past events
 - ▶ Repeating a sequence of inputs always gives the same output sequence
- ▶ **Sequential logic (covered later) does have memory**
 - ▶ Repeating a sequence of inputs can result in an entirely different output sequence

Design Hierarchy

- ▶ Large systems are usually too complex to design as a single entity
 - ▶ i.e., a 16 bit binary adder has 32 inputs and therefore there are 2^{32} rows in the truth table!
- ▶ System is usually partitioned into smaller parts which are further partitioned ...
- ▶ This defines a hierarchy of design from complex to simple;
 - ▶ “top to bottom”

Design Methodologies

- ▶ There are two basic approaches to system design
 - ▶ Top-Down: start at the top system level and decompose into ever simpler subsystems and components
 - ▶ Bottoms-Up: start with known low-level building blocks and put them together into increasing complex functions
- ▶ Ideally either should work; however, in practice neither method does

Concurrent Design

- ▶ The practical approach is to combine the two
 - ▶ Basic top-down to provide proper decomposition and validation
 - ▶ BUT as you decompose functions, be aware of:
 - ▶ already existing and available components
 - ▶ component to component interface characteristics
 - ▶ reality - cost, size, weight, power, etc.
- ▶ If done properly, you end up with a low-cost practical solution that works!

Rapid Prototyping and CAD

- ▶ Design verification is much more difficult with VLSI ASICs than with SSI designs
 - ▶ Lots more signals and less accessibility
- ▶ Rapid prototyping assumes we can build many different versions and see which ones work
 - ▶ Programmable logic is vital to this approach
 - ▶ Good development tools are also essential
- ▶ Hardware description languages are the way we quickly specify and change our designs

Hardware Description Languages (HDLs)

- ▶ Two main HDLs in use today
 - ▶ VHDL
 - ▶ Verilog
- ▶ Both are IEEE standards
- ▶ Both allow us to specify logic designs as textual descriptions
 - ▶ BE AWARE - both look like a software procedure but are describing HARDWARE!
 - ▶ Concurrency!!!
- ▶ We will use Verilog

Logic Synthesis

- ▶ Logic synthesis translates the HDL to our hardware implementation
 - ▶ 1st phase translates HDL to a generic, ideal logic description
 - ▶ logic expressions generated and minimized
 - ▶ allows us to verify functional operation
 - ▶ 2nd phase targets the design to the final physical device
 - ▶ complexity, speed, delays, power must be addressed
 - ▶ we can now simulate physical operation of device

Digital Logic Implementation

- ▶ Circuit Properties: logic representation, size, weight, power, package, temperature, COST
- ▶ Levels of Integration: ranges from small scale ICs with a few basic gates per package to VLSI devices containing millions of gates per package
- ▶ Circuit Technology: TTL, ECL, CMOS, GaAs, SiGe, etc.

Technology Parameters

- ▶ Fan-in
- ▶ Fan-out
- ▶ Noise margin
- ▶ Propagation delay
- ▶ Power dissipation

Fan-In

- ▶ For logic gates, it's the max number of inputs to a specific gate
 - ▶ Defined by gate design; usually limited to a max of 4 or 5
 - ▶ E.G. 74LS08 is a Quad, 2-input AND device
 - ▶ 4 AND gates in package, each AND has 2 inputs
- ▶ Primary impact is when you have more variables than your gate has input
 - ▶ Cascade gates, transform function, etc.

Fan-Out

- ▶ Fan-out is usually defined as the max number of “standard” logic gate inputs that can be connected to a logic gate output
 - ▶ Specifies the “drive” capability of an output
- ▶ If an output is overloaded, other characteristics such as noise margin, rise & fall times are degraded
- ▶ Different logic types are affected by “overload” in different ways

Noise Margin

- ▶ Noise Margin defines how much noise can be induced onto a logic signal and still be correctly recognized as a high or low level
- ▶ Difference between output high or low level and input level that will be recognized as high or low

TTL
Logic
Levels

$$V_{oh} = 2.8 \text{ v}$$

$$V_{ih} = 2.4 \text{ v}$$

$$V_{il} = 0.8 \text{ v}$$

$$V_{ol} = 0.4 \text{ v}$$

Noise margin high = 0.4 v

Transition region; neither Hi or Lo!

Noise margin low = 0.4 v

Propagation Delay

- ▶ Real devices do not have zero delay!
- ▶ Propagation delays are measured from input change to output change (tPD)
 - ▶ Usually referenced to 50% point on transition
- ▶ Gates usually have different delays for the output low to high (tLH) and high to low (tHL)
- ▶ Best to design using the max of the two
- ▶ Not all input changes show up at the output
 - ▶ Gate may not respond to a narrow pulse

Power Dissipation

- ▶ The quantity of electrical power that is dissipated by the device as heat
 - ▶ Devices have temperature operating range that device cannot exceed
- ▶ Power dissipation is mainly static or dynamic depending on the logic type
 - ▶ TTL/ECL dissipation is mainly static and therefore independent of signal rate of change
 - ▶ CMOS dissipation is mainly dynamic and increases linearly with increasing signal freq.


Signal Active States and Bubbles

- ▶ Primarily applies to control signals; used to denote when a condition is active or enabled
 - ▶ Active State - signal state (0 or 1) that indicates the assertion of some condition or action
 - ▶ Also called the excitation state
 - ▶ A signal is asserted when it is in the active state
 - ▶ A signal is negated when it is in the inactive state
 - ▶ Active-1 (active high) is when active state is logic 1
 - ▶ Active-0 (active low) is when active state is logic 0
 - ▶ Symbol pins without bubbles denote active-1
 - ▶ Symbol pins with bubbles denote active-0

Active States and Bubbles (Cont'd.)


- ▶ Inverter (NOT) has two different forms

Input asserted
active-1

 

Output asserted
active-0

Input asserted
active-0

 

Output asserted
active-1

Alternative Symbols


- ▶ The NOT example can be extended to all logic gates
 - ▶ Each logic gate has two equivalent symbols
 - ▶ The one we've seen so far for active-1 inputs
 - ▶ The alternate for active-0 inputs
 - ▶ In each case the gate operates the same
 - ▶ The only difference is how we interpret the values

AND Gate Alternate Symbol

X	Y	X·Y
0	0	0
0	1	0
1	0	0
1	1	1


Active-1

X	Y	X·Y
F	F	F
F	T	F
T	F	F
T	T	T

 

Active-0

X	Y	X+Y
T	T	T
T	F	T
F	T	T
F	F	F

 


OR Gate Alternate Symbol

X	Y	X+Y
0	0	0
0	1	1
1	0	1
1	1	1


Active-1

X	Y	X+Y
F	F	F
F	T	T
T	F	T
T	T	T

 

Active-0

X	Y	X·Y
T	T	T
T	F	F
F	T	F
F	F	F


 


Other Gate Alternative Symbols



Active-1

Active-0



NAND

  



NOR

  

XOR

  

XNOR

 
 


Signal Naming Conventions

- ▶ The problem is how to distinguish between active-1 and active-0 signals.
 - ▶ Barring a signal name to designate active-0 is not recommended
 - ▶ Is A active-0 or NOT A?? \overline{A}
 - ▶ Use suffix of ‘_0’; (i.e A_0) after signal name
 - ▶ Use suffix of ‘_LO’ or ‘_L’
 - ▶ Use suffix of ‘_BAR’
- ▶ No matter what you use, BE CONSISTENT!

Signal Naming (Cont'd.)

 
 
- ▶ Active-0 signal naming and symbol bubbles require some thought to interpret properly



Naming and Alternate Symbols

- ▶ Proper active-0 signal naming and usage of alternate symbols can clarify the circuit intent
  
$$\text{HEAT} = \text{TEMP1_L} \cdot \text{TEMP2_L}$$



Design Methodology

- ▶ We start with some form of a problem statement
 - ▶ Usually just text; ambiguous, poorly stated
- ▶ We must produce a design representation
 - ▶ S.A. expressions, minimized
- ▶ The primary problem we have, is first to concisely define the true problem we are to solve
 - ▶ Define the “system” requirements

Design Methodology (Cont'd.)

- ▶ Step 1 - Break down the problem statement
 - ▶ Identify system inputs and outputs
 - ▶ Extract the stated input-output relationship(s)
 - ▶ State the above as system (black-box) level requirements. BE PRECISE!

- ▶ Step 2 - Perform initial system definition
 - ▶ Define interface variables and representation
 - ▶ If representation is not defined in problem statement, make preliminary assignment
 - ▶ Restate I/O relationship as algorithm, equation, simulation, etc.

Design Methodology (Cont'd.)


- ▶ Step 3 - Translate relationships to logic representation
 - ▶ Construct truth table, generate S.A. expressions
 - ▶ This is the formal statement of the I/O relationship(s)
- ▶ Step 4 - Generate minimal set of logic expressions
 - ▶ Rapid prototyping development tools
 - ▶ Karnaugh maps, Quine-McCluskey, etc.

Design Methodology (Cont'd.)

- ▶ Step 5 - Implement and verify the design
 - ▶ Rapid prototyping (programmable logic) - target device and simulate timing behavior
 - ▶ Otherwise, draw schematic
 - ▶ Lots of ways to actually implement the equations
 - ▶ Must know what logic family you are to use.
 - ▶ Acid test is to build the circuit and test it
 - ▶ Must operate in real-world environment
 - ▶ Noise, temperature, other factors may cause problems

BCD to XS3 Example

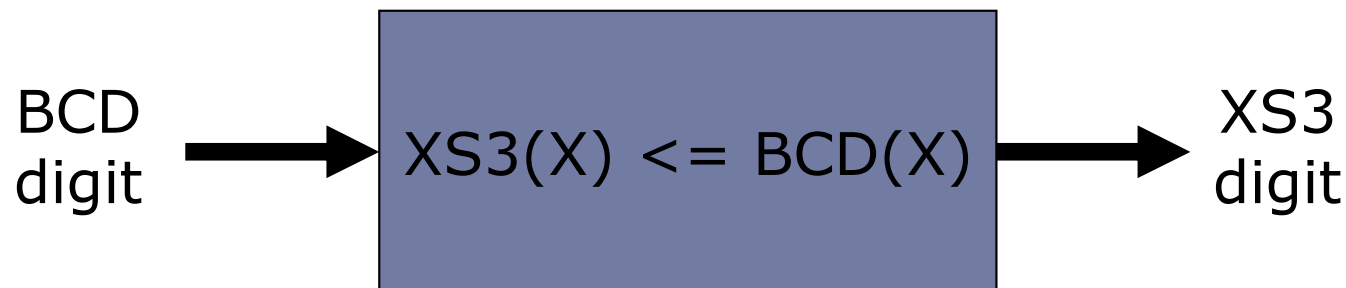- ▶ Initial Statement: “Design a circuit to convert BCD to XS3.”
 - ▶ 1) We need to restate and translate this to specific requirements
 - ▶ R1: The circuit shall input one BCD digit
 - ▶ R2: The circuit shall output one XS3 digit
 - ▶ R3: The XS3 output shall be the equivalent decimal value as the BCD input value



BCD to XS3 Example (Cont'd.)

- ▶ 2) Now we need to define the interfaces in detail
 - ▶ We know that the input is one decimal digit in BCD representation, i.e. 4 bits, $\text{BCD} := \{b_3, b_2, b_1, b_0\}$
 - ▶ The output is one XS3 decimal digit, which is also 4 bits, i.e. $\text{XS3} := \{x_3, x_2, x_1, x_0\}$
 - ▶ Usually, well known representations don't need explicit definition; when in doubt, DEFINE IT!

- ▶ 3) Now we use a truth table to define the logical input/output relationship
 - ▶ Only 10 of 16 possible input combinations are valid
 - ▶ We'll assume last 6 won't occur; i.e. are don't cares

BCD to XS3 Example (Cont'd.)

b_3	b_2	b_1	b_0	x_3	x_2	x_1	x_0
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	-	-	-	-
1	0	1	1	-	-	-	-
1	1	0	0	-	-	-	-
1	1	0	1	-	-	-	-
1	1	1	0	-	-	-	-
1	1	1	1	-	-	-	-

Note: Don't cares can work to our advantage during minimization; we can assign either 0 or 1 as needed.

BCD to XS3 Example (Cont'd.)

- ▶ 4) Now we can generate the logical expressions for the outputs (canonical SofP form)

$$x_3 = \overline{b_3}\overline{b_2}\overline{b_1}b_0 + \overline{b_3}\overline{b_2}b_1\overline{b_0} + \overline{b_3}\overline{b_2}b_1b_0 + b_3\overline{\overline{b_2}\overline{b_1}\overline{b_0}} + b_3\overline{\overline{b_2}\overline{b_1}b_0}$$

$$x_2 = \overline{\overline{b_3}\overline{b_2}\overline{b_1}b_0} + \overline{\overline{b_3}\overline{b_2}b_1\overline{b_0}} + \overline{\overline{b_3}\overline{b_2}b_1b_0} + \overline{b_3\overline{\overline{b_2}\overline{b_1}\overline{b_0}}} + \overline{b_3\overline{\overline{b_2}\overline{b_1}b_0}}$$

$$x_1 = \overline{\overline{b_3}\overline{b_2}\overline{b_1}b_0} + \overline{\overline{b_3}\overline{b_2}b_1\overline{b_0}} + \overline{\overline{b_3}\overline{b_2}\overline{b_1}b_0} + \overline{b_3\overline{\overline{b_2}\overline{b_1}\overline{b_0}}} + \overline{b_3\overline{\overline{b_2}\overline{b_1}b_0}}$$

$$x_0 = \overline{\overline{b_3}\overline{b_2}\overline{b_1}b_0} + \overline{\overline{b_3}\overline{b_2}b_1\overline{b_0}} + \overline{\overline{b_3}\overline{b_2}\overline{b_1}b_0} + \overline{b_3\overline{\overline{b_2}\overline{b_1}\overline{b_0}}} + \overline{b_3\overline{\overline{b_2}\overline{b_1}b_0}}$$

BCD to XS3 Example (Cont'd.)

- ▶ The minimized equations are as follows:


$$X_3 = b_3 + b_2b_1 + b_2b_0$$

$$X_2 = \overline{b_2}b_1 + \overline{b_2}b_0 + b_2\overline{b_1}\overline{b_0}$$

$$X_1 = \overline{b_1}\overline{b_0} + b_1b_0 = \overline{b_1 \oplus b_0}$$

$$x_0 = \overline{b_0}$$

BCD to XS3 Example (Cont'd.)

 

Technology Mapping

- ▶ Translation of out “ideal” circuit design to actual hardware must account for the implementation method
 - ▶ ASICs: full custom, standard cell, or gate arrays
 - ▶ Programmable logic: FPGAs or PLDs
 - ▶ Gate types, input configurations available
- ▶ Vendors supply you with a set of logic gate design patterns known as a cell library
 - ▶ Defines implementation rules as well as gate types
- ▶ CAD tools then use the provided library to map the ideal design to the physical implementation
 - ▶ Translates design to preferred logic types

-
- ▶ Checks for problems, fanout, propagation times exceeded

Verification

- ▶ Ensuring that the final device actually works is mandatory and can also be hard to do
- ▶ Must start with good requirements (validation)
 - ▶ It's really bad to find out your design meets the stated requirements but it's not what the customer wanted
- ▶ Done at different stages of the development
 - ▶ Simulation used during the design capture and implementation mapping phase
 - ▶ Functional and parametric testing after device fabrication