

Fall 2016 BSM 203 Logic Circuits Final Exam Solutions

1. For the circuit given in the work sheet, answer the following questions.

a. Derive the FF input equations (D, T), FF next state equations (A^+ and B^+), and output equation (Z).

$$D = X'F_1 + XF_2 = X'(X+B) + X(X'A) = X'B \quad T = D' = X + B'$$

$$A^+ = D = X'B \quad B^+ = T'B + TB' = (X'B)B + (X+B')B' = X'B + XB' + B' = X'B + B' = X' + B'$$

$$Z = m_1 = AB'(X'B' + XB) = X'AB'$$


b. Is this a Mealy Machine or Moore Machine? Explain your answer in one sentence below.

This is a Mealy machine, because output depends on both the input and FF outputs.


c. Construct the state transition table, next state table, and state graph below.

Next-State Table				
AB	A^+B^+		Z	
	X=0	X=1		
00	01	01	0	0
01	11	00	0	0
11	11	00	0	0
10	01	01	1	0

State-Transition Table					
Present	Next		Output		
	X=0	X=1			
S_0	S_1	S_1	0	0	
S_1	S_2	S_0	0	0	
S_2	S_2	S_0	0	0	
S_3	S_1	S_1	1	0	

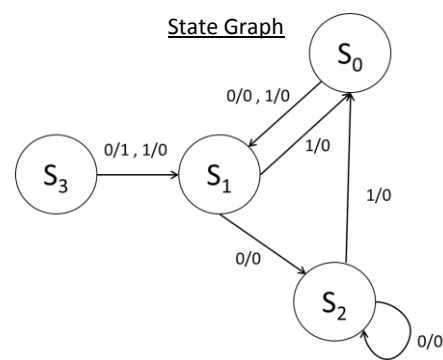


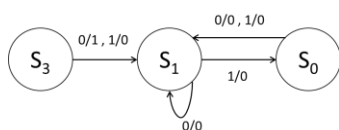As you may notice, S_1 and S_2 are equivalent states. Thus we can remove S_2 , then the state graph is below:



Whoever notice this will get 5 bonus points.

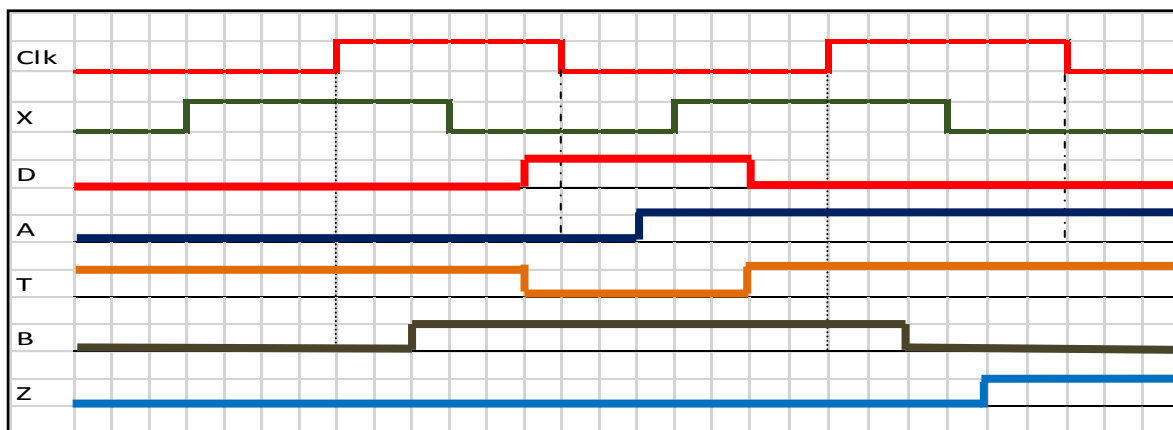
d. Complete the timing chart shown below for the circuit for an input sequence X as shown in the chart below and the clock period 12ns. Assume that T-FF is rising-edge and D-flip flop is falling-edge triggered, that initially $A = B = 0$, and that X changes midway between the rising and falling clock edges. The delays in ROM, decoder, and MUX are 1 ns for each and delay in each FF is 2 ns. The delay in XOR gate is negligible.



2. Please indicate which question you solved (2.1 or 2.2): **2.1** (This is basically a sequence detector for either 011 or 110.

For Mealy Machine

Step 1: Derive the state graph

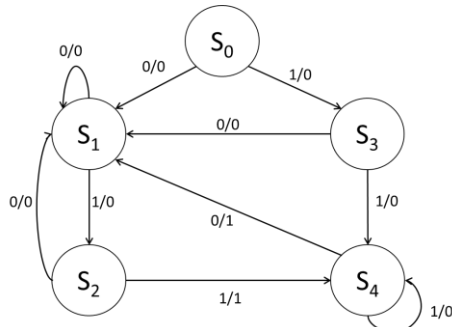

Step 2: Construct state-transition table

State-Transition Table				
Present	Next State		Z	
	X = 0	X = 1	X = 0	X = 1
S ₀	S ₁	S ₃	0	0
S ₁	S ₁	S ₂	0	0
S ₂	S ₁	S ₄	0	1
S ₃	S ₁	S ₄	0	0
S ₄	S ₁	S ₄	1	0

Step 3: Decide how many FFs required and construct next-state table

Next-State Table				
ABC	A ⁺ B ⁺ C ⁺		Z	
	X = 0	X = 1	X = 0	X = 1
000	001	011	0	0
001	001	010	0	0
010	001	100	0	1
011	001	100	0	0
100	001	100	1	0

Step 4: Decide the type of FF you use and derive the FF input equations and output equation.

$$Z = X'A + XBC'$$

For D Flip-Flop: $D_A = X(A + B)$; $D_B = XA'B'$; $D_C = X' + A'B'C'$


For T Flip-Flop: $T_A = X'A + XB$; $T_B = A + (X+B)$; $T_C = (X \oplus C)' + A'B'C'$

For J-K FF: $J_A = XB$ $K_A = X'$ (or B) $J_B = XA'$ $K_B = 1$ $J_C = X' + B'$ $K_C = 1$

Surely in answers, just equations are not sufficient, Karnaugh maps should be here as well.

For Moore Machine

Step 1: Derive the state graph

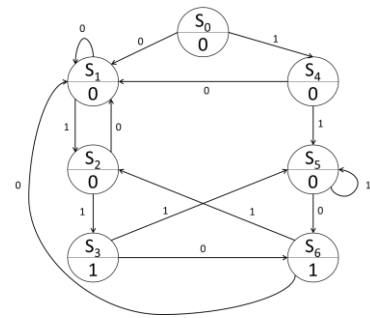

Step 2: Construct state-transition table

State-Transition Table			
Present	Next State		Z
	X = 0	X = 1	
S ₀	S ₁	S ₄	0
S ₁	S ₁	S ₂	0
S ₂	S ₁	S ₃	0
S ₃	S ₆	S ₅	1
S ₄	S ₁	S ₅	0
S ₅	S ₆	S ₅	0
S ₆	S ₁	S ₂	1

Step 3: Decide how many FFs required and construct next-state table

Next-State Table			
ABC	A ⁺ B ⁺ C ⁺		Z
	X = 0	X = 1	
000	001	100	0
001	001	010	0
010	001	011	0
011	110	101	1
100	001	101	0
101	110	101	0
110	001	010	1

Step 4: Decide the type of FF you use and derive the FF input equations and output equation.

$$Z = A'BC + ABC' = B(A \oplus C)$$

For D Flip-Flop: $D_A = C(A + B) + X'B'C'$; $D_B = X(B'C' + A'B'C) + X'C(A + B)$; $D_C = X'(C' + A'B') + A(X \oplus B)$

For T Flip-Flop: $T_A = B(A + C) + C'(XA'B' + X'A)$; $T_B = C(X \oplus A) + X'BC$; $T_C = X'(A + C) + C'(A \oplus B) + XA'B'C$


For J-K FF: $J_A = BC + X'B'C'$ $K_A = B + X'C'$ $J_B = C(X \oplus A)$ $K_B = (X \oplus C)'$ $J_C = X' + (A \oplus B)$ $K_C = X \oplus (A + B)$

Surely in answers, just equations are not sufficient, Karnaugh maps should be here as well.

2. Please indicate which question you solved (2.1 or 2.2): **2.2 sequence detector for 0010.**

For Mealy Machine

Step 1: Derive the state graph

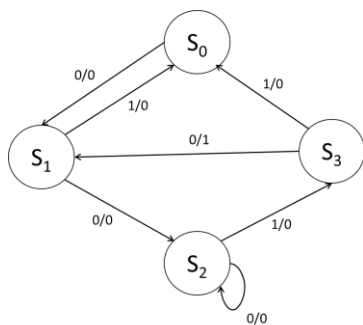

Step 2: Construct state-transition table

State-Transition Table				
Present	Next State		Z	
	X = 0	X = 1	X = 0	X = 1
S ₀	S ₁	S ₀	0	0
S ₁	S ₂	S ₀	0	0
S ₂	S ₂	S ₃	0	0
S ₃	S ₁	S ₀	1	0

Step 3: Decide how many FFs required and construct next-state table

Next-State Table				
AB	A ⁺ B ⁺		Z	
	X = 0	X = 1	X = 0	X = 1
00	01	00	0	0
01	11	00	0	0
11	11	10	0	0
10	10	00	1	0

Step 4: Decide the type of FF you use and derive the FF input equations and output equation.

$$Z = X'AB'$$

For D Flip-Flop: $D_A = B(X' + A)$; $D_B = X'$;


For T Flip-Flop: $T_A = AB' + X'A'B$; $T_B = (X \oplus B)'$;

For J-K FF: $J_A = X'B$ $K_A = B'$ $J_B = X'$ $K_B = X$

Surely in answers, just equations are not sufficient, Karnaugh maps should be here as well.

For Moore Machine

Step 1: Derive the state graph

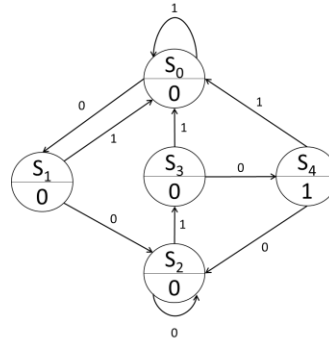

Step 2: Construct state-transition table

State-Transition Table			
Present	Next State		Z
	X = 0	X = 1	
S ₀	S ₁	S ₀	0
S ₁	S ₂	S ₀	0
S ₂	S ₂	S ₃	0
S ₃	S ₄	S ₀	0
S ₄	S ₂	S ₀	1

Step 3: Decide how many FFs required and construct next-state table

Next-State Table			
ABC	A ⁺ B ⁺ C ⁺		Z
	X = 0	X = 1	
000	001	000	0
001	010	000	0
010	010	011	0
011	100	000	0
100	010	000	1

Step 4: Decide the type of FF you use and derive the FF input equations and output equation.

$$Z = AB'C'$$

For D Flip-Flop: $D_A = X'BC$; $D_B = BC' + X'(A + B'C)$;
 $D_C = C'(X'A'B' + XB)$

For T Flip-Flop: $T_A = A + X'BC$ $T_B = BC + X'(A + B)$
 $T_C = C + XB + X'A'B'$

For J-K FF: $J_A = X'BC$ $K_A = 1$ $J_B = X'(A + C)$ $K_B = C$
 $J_C = X'A'B' + XB$ $K_C = 1$

Surely in answers, just equations are not sufficient, Karnaugh maps should be here as well.